

Introduction to Data Acquisition System

Tassadaq Hussain Cheema
Professor NAMAL University
Pakistan Supercomputing Center
Barcelona Supercomputing Center


Agenda

- Introduction
- DAS Blocks
- Characteristic Values of ADCs
- Nyquist-Rate ADCs
- Oversampling ADC
- Practical Issues
- Low Power ADC Design


Introduction

- ADC = **A**nalog-**D**igital-**C**onverter
- Conversion of **audio** signals (mobile micro, digital music records, ...)
- Conversion of **video** signals (cameras, frame grabber, ...)
- **Measured value acquisition** (temperature, pressure, luminance, ...)


ADC - Scheme

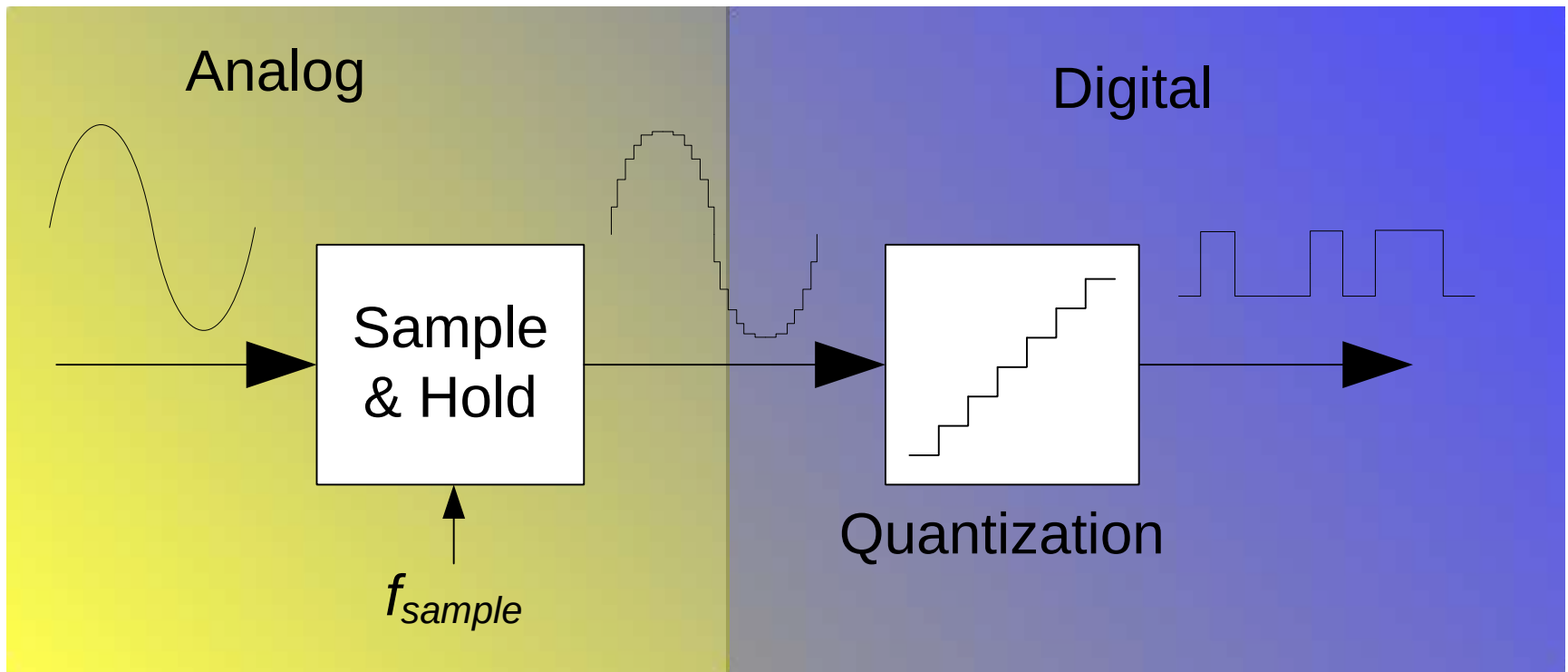


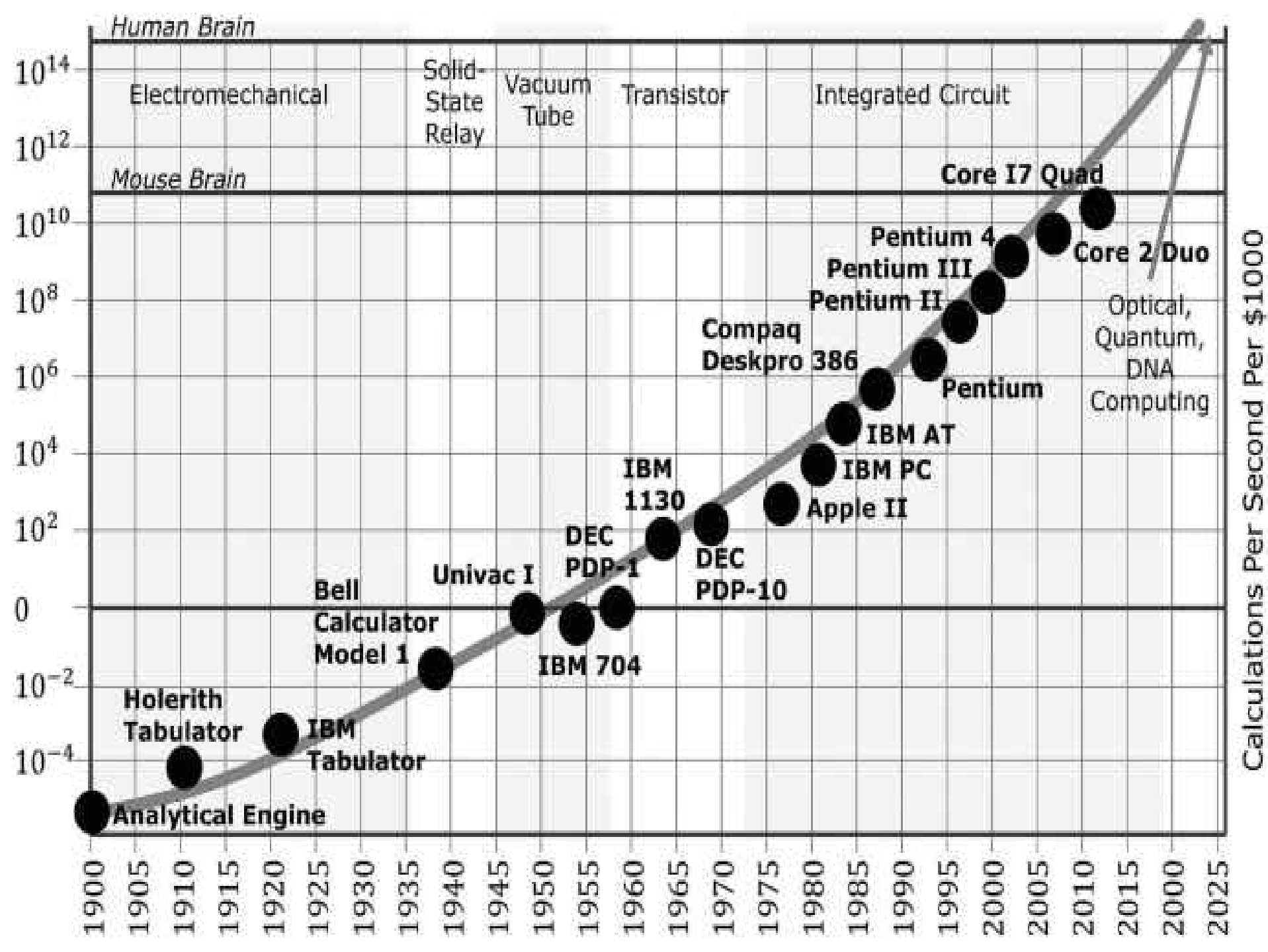- Analog input can be voltage or current (*in the following only voltage*)
- Analog input can be positive or negative (*in the following only positive*)



Volume in Exabytes

 


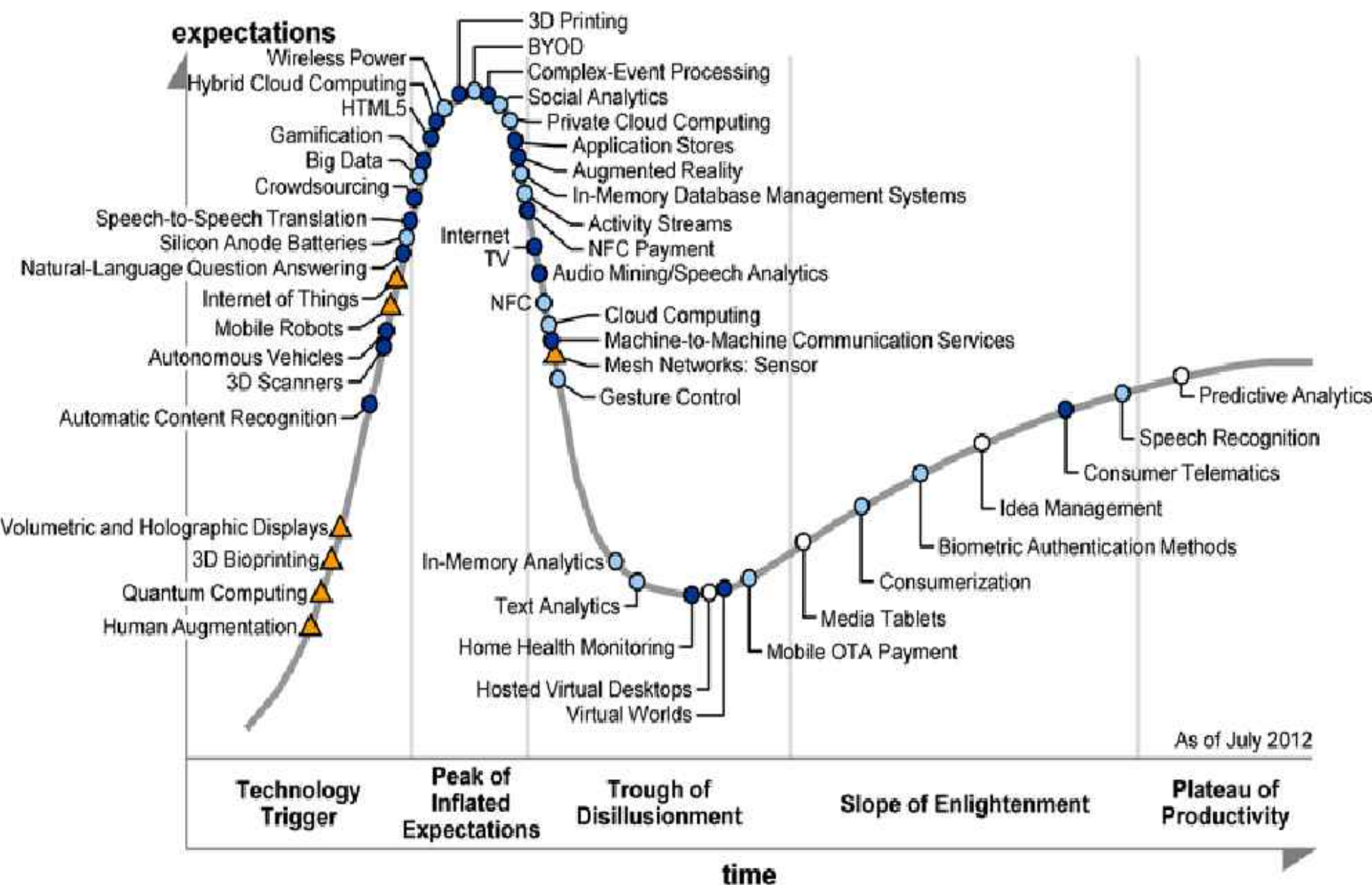


Plateau will be reached in:

- less than 2 years
- 2 to 5 years
- 5 to 10 years
- ▲ more than 10 years
- ⊗ obsolete before plateau

Figure 1: Gartner Hype cycle ^[11]

Big Data

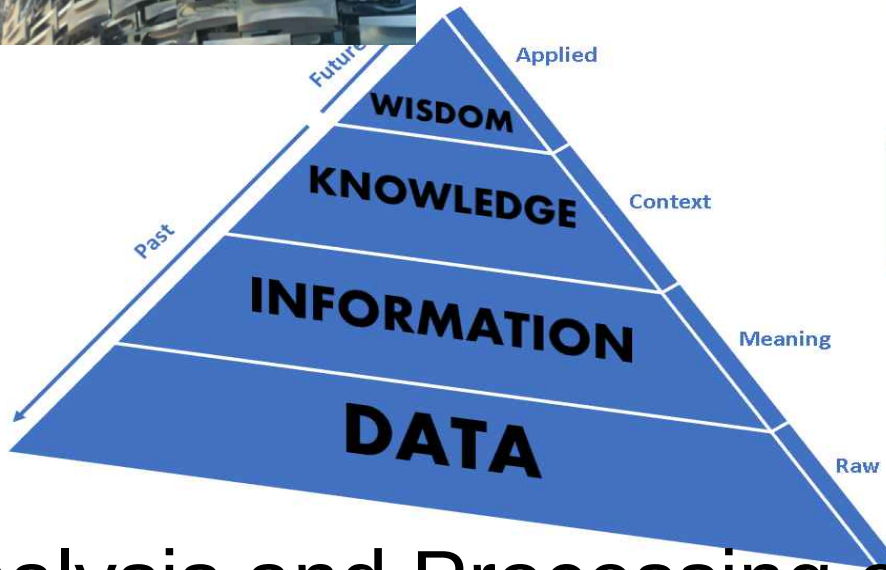 

Analysis and Processing of Big Data are changing the energy market map


DAS



Figure 3 Interfaced with variety of SBC

Stages of DAS

 - Signal Conditioning
 - To improve the quality of signals in terms of amplification, linearization, compensation, filtering, and attenuation.
- Buffering
- Amplification
- Multiplexing
- ADC



2. Characteristic Values of ADCs


- Which values characterize an ADC?
- What kind of errors exist?
- What is aliasing?

ADC Values

- **Resolution N:** number of discrete values to represent the analog values (in Bit)
 - 8 Bit = $2^8 = 256$ quantization level,
 - 10 Bit = $2^{10} = 1024$ quantization level
- **Reference voltage V_{ref} :** Analog input signal V_{in} is related to digital output signal D_{out} through V_{ref} with:

$$V_{in} = V_{ref} \cdot (D_0 2^{-1} + D_1 2^{-2} + \dots + D_{N-1} 2^{-N})$$

 - Example: $N = 3$ Bit, $V_{ref} = 1V$, $D_{out} = '011'$
 $\Rightarrow V_{in} = 1V \cdot (2^{-2} + 2^{-3}) = 1V \cdot (0.25 + 0.125) = 0.375V$



ADC Values cont'd

- V_{LSB} : Minimum measurable voltage difference in ideal case (LSB – least significant Bit)
 - $V_{LSB} = V_{ref} / 2^N$
 - $V_{in} = V_{LSB} (D_0 2^{N-1} + D_1 2^{N-2} + \dots + D_{N-1} 2^0)$
 - Example: $N = 3$ Bit, $V_{ref} = 1V$, $D_{out} = '011'$
 - $\Rightarrow V_{LSB} = 1V / 2^3 = 0.125V$
 - $\Rightarrow V_{in} = 0.125V \cdot (2^1 + 2^0) = 0.125V \cdot 3 = 0.375V$
- ΔV : Voltage difference between two logic level
 - Ideal: all $\Delta V = V_{LSB}$
- V_{FSR} : Difference between highest and lowest measurable voltages (FSR – full scale range)

ADC Values cont'd

- **SNR:** Signal to Noise Ratio

- Ratio of signal power to noise power

- $SNR = \frac{P_{signal}}{P_{noise}}$, $SNR|_{db} = 10 \log \left(\frac{P_{signal}}{P_{noise}} \right)$


- **ENOB:** Effective Number of Bits

- Effective resolution of ADC under observance of all noise and distortions

- **SINAD** (Signal to Noise And Distortion) → ratio of fundamental signal to the sum of all distortion and noise (DC term removed)

- Comparison of SINAD of ideal and real ADC with same word length


Ideal ADC

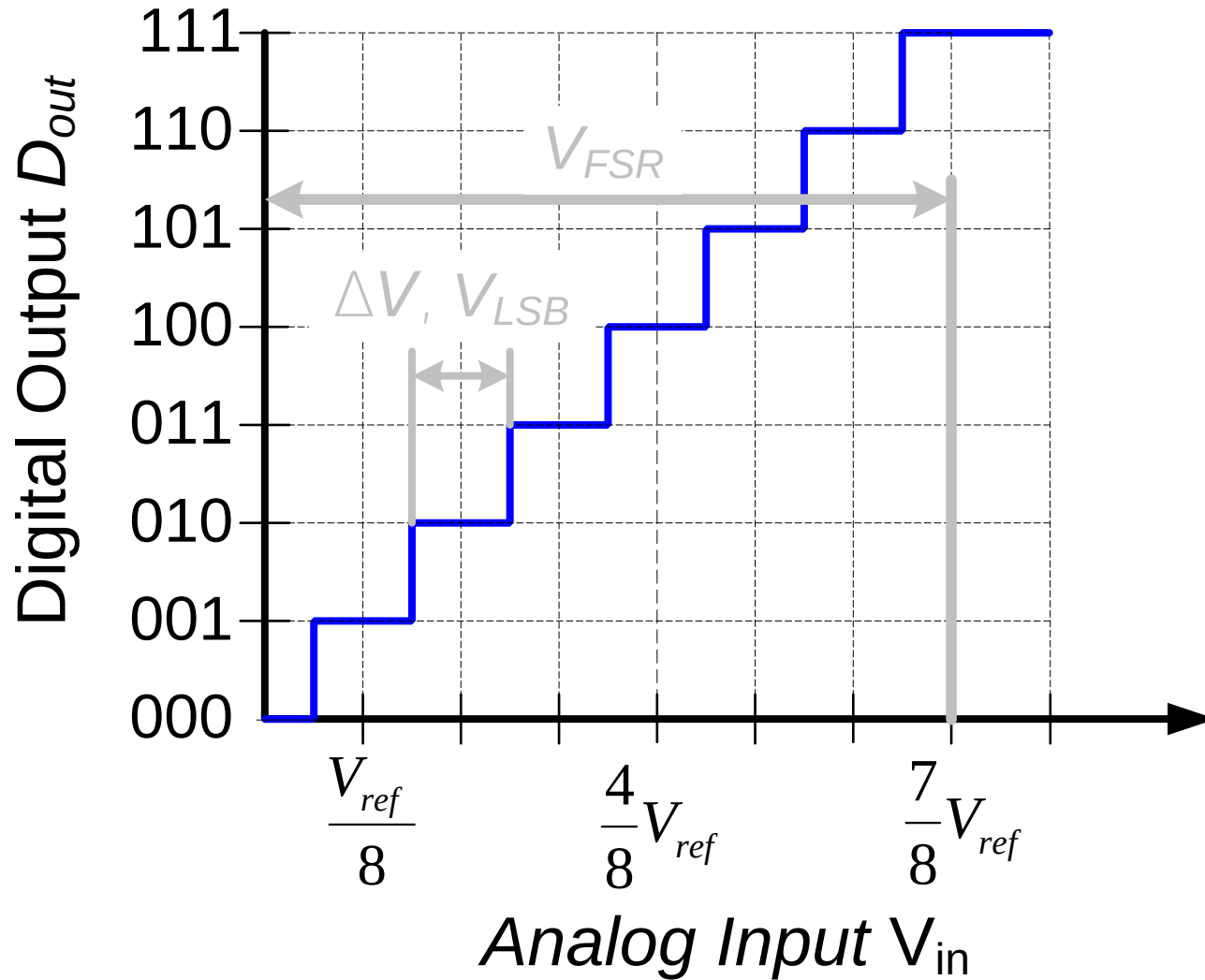


Further ADC Values

- **Bandwidth:** Maximum measurable frequency of the input signal
- **Power dissipation**
- **Conversion Time:** Time for conversion of an analog value into a digital value (*interesting in pipeline and parallel structures*)
- **Sampling rate (f_{samp}):** Rate at which new digital values are sampled from the analog signal (also: sample
- **Errors:** Quantization, offset, gain, INL, DNL, missing codes, non-monotonicity...

Quantization Error ϵ

 


Offset Error

 


- Parallel shift of the whole curve
- E.g. caused by difference in ground line voltages

Gain Error

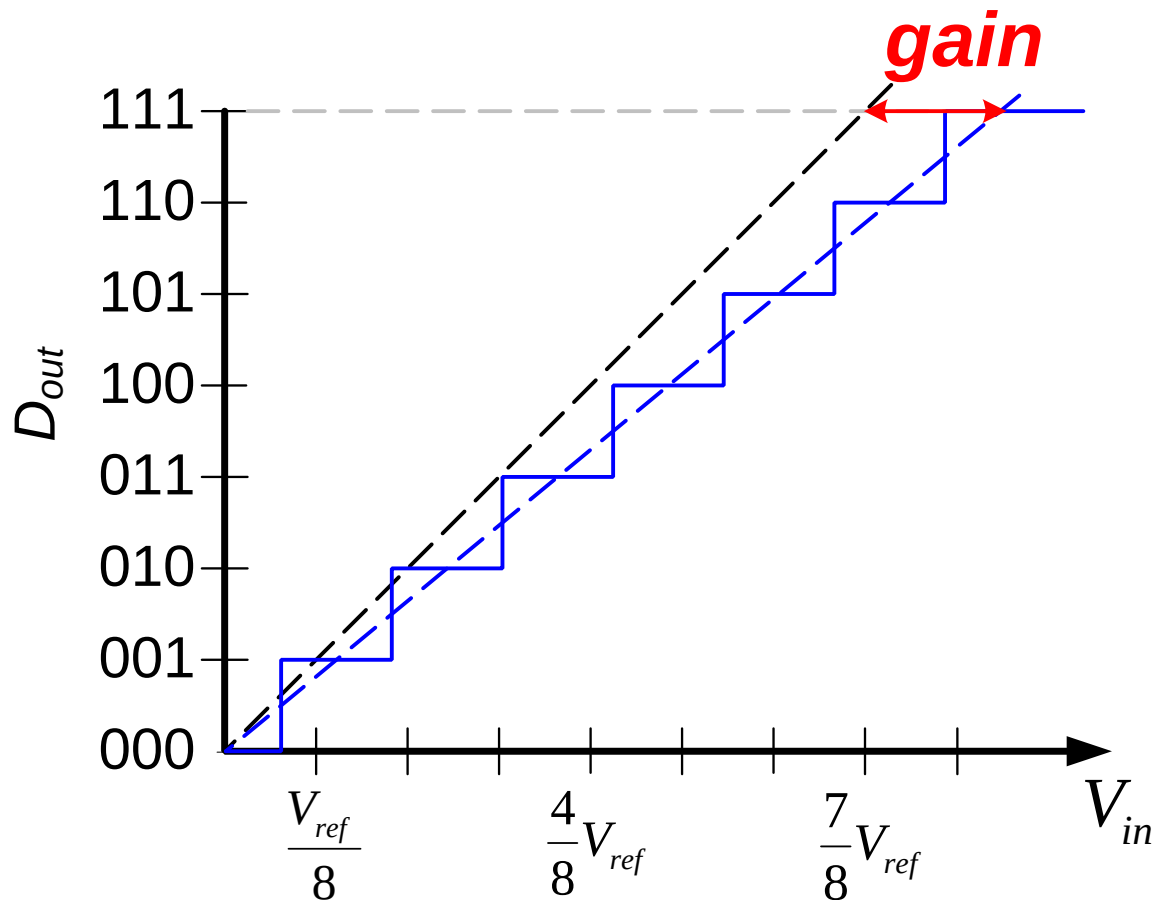


- Corresponds to too small or too large but equal ΔV
- E.g. caused by too small or too large V_{ref}

Differential Non-Linearity (DNL)

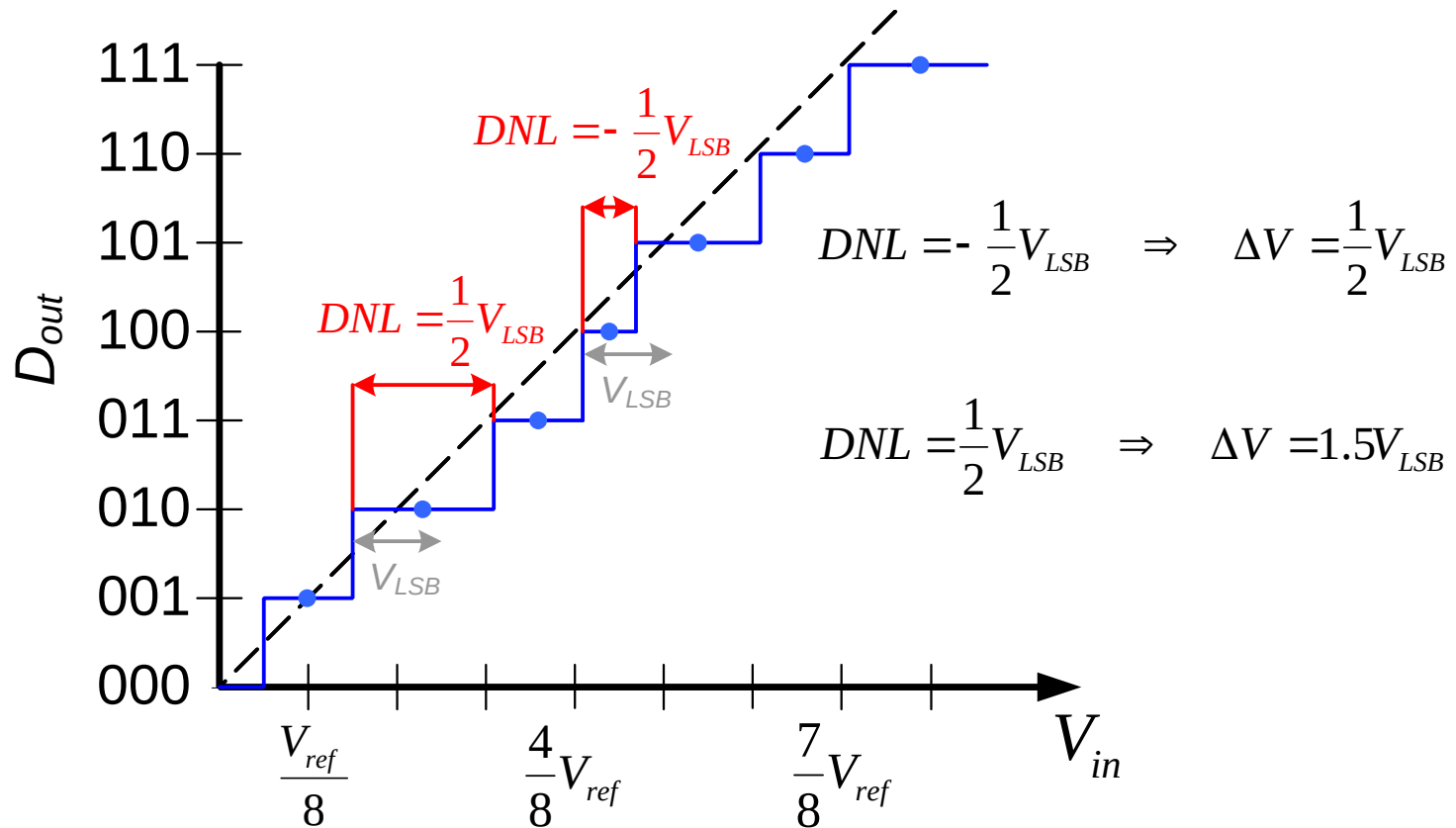


- Deviation of ΔV from V_{LSB} value (in V_{LSB})
- Defined after removing of gain
- E.g. Caused by mismatch of the reference elements

Missing Codes

 


- Some bit combinations never appear
- Occurs, if maximum $DNL > 1 V_{LSB}$ or maximum $INL > 0.5 V_{LSB}$

Non-Monotonicity

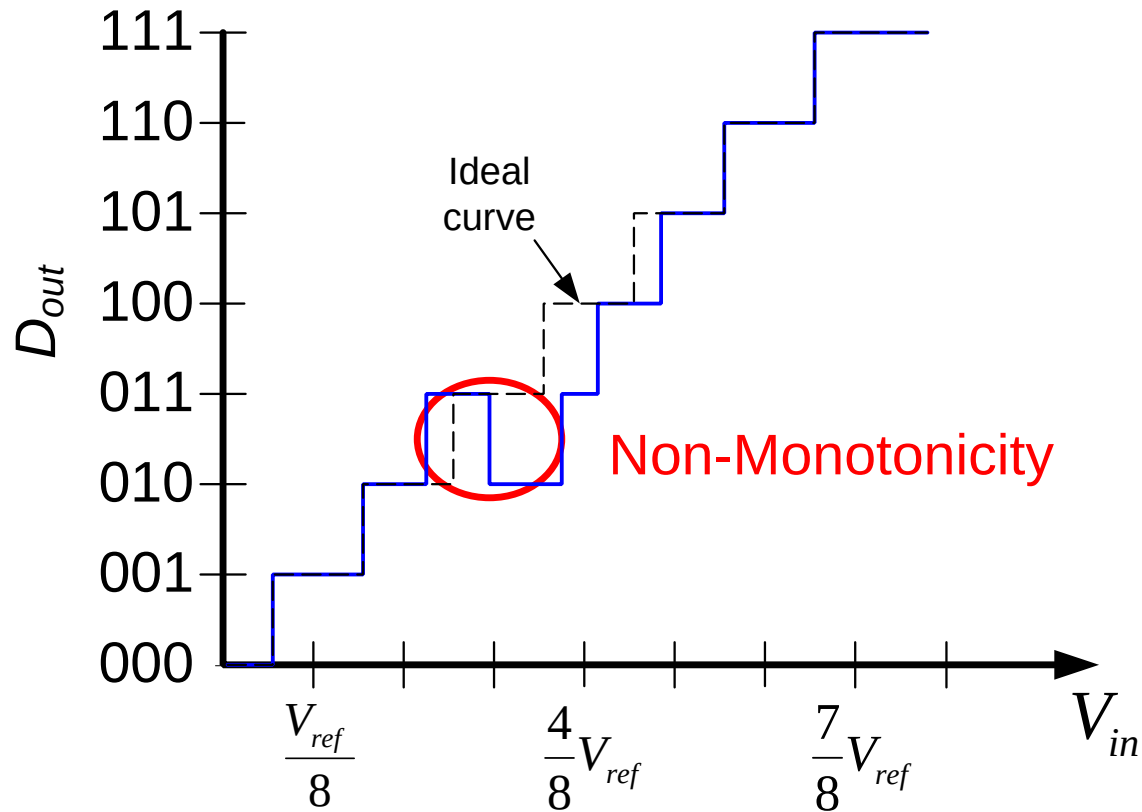

- Lower conversion result for a higher input voltage
- Includes that same conversion may result from two separate voltage ranges

Aliasing

 

- Too small sampling rate f_{samp} (under-sampling) can lead to **aliasing** (= frequency of reconstructed signal is too low)
- Nyquist criterion:
 - f_{samp} more than **two times higher** than highest frequency component f_{in} of input signal: $f_{samp} > 2 \cdot f_{in}$

3. Nyquist-Rate ADCs


- How can Nyquist-rate ADCs be grouped?
- What is a dual slope ADC?
- What is a successive approximation ADC?
- What is an algorithmic ADC?
- What is a flash ADC?
- What is a pipelined ADC?
- What are the pros and cons of the Nyquist-rate ADCs?

Nyquist-Rate ADCs



- Sampling frequency f_{smp} is in the same range as frequency f_{in} of input signal
- Low-to-medium speed and high accuracy ADCs
 - Integrating
- Medium speed and medium accuracy ADCs
 - Successive Approximation
 - Algorithmic
- High speed and low-to-medium accuracy ADCs
 - Flash
 - Two-Level Flash
 - Pipelined

Successive Approximation ADC

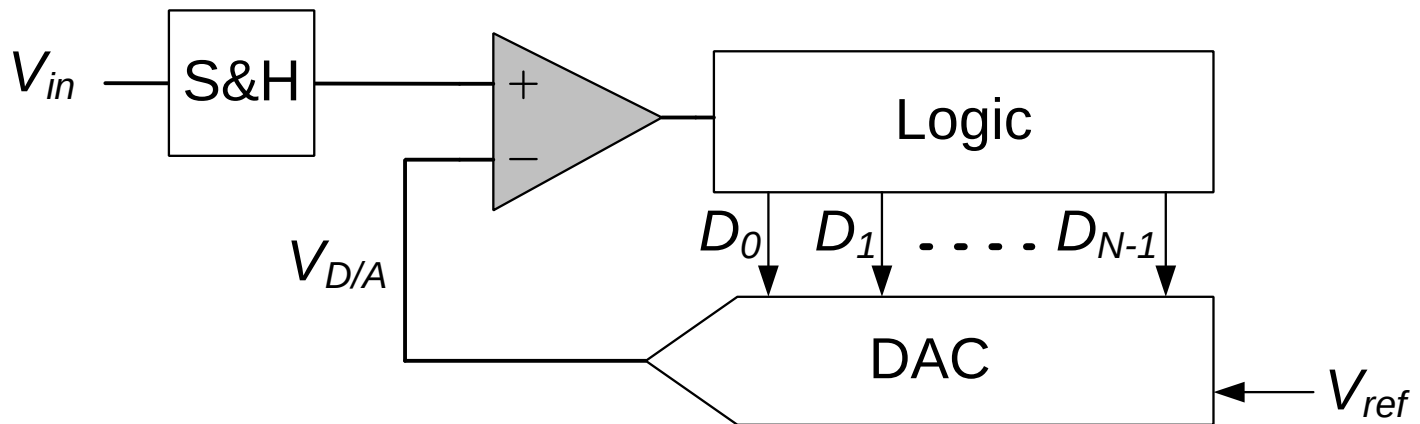
- Generate internal analog signal $V_{D/A}$
- Compare $V_{D/A}$ with input signal V_{in}
- Modify $V_{D/A}$ by $D_0D_1D_2\dots D_{N-1}$ until closest possible value to V_{in} is reached



Successive Approximation ADC cont'd

 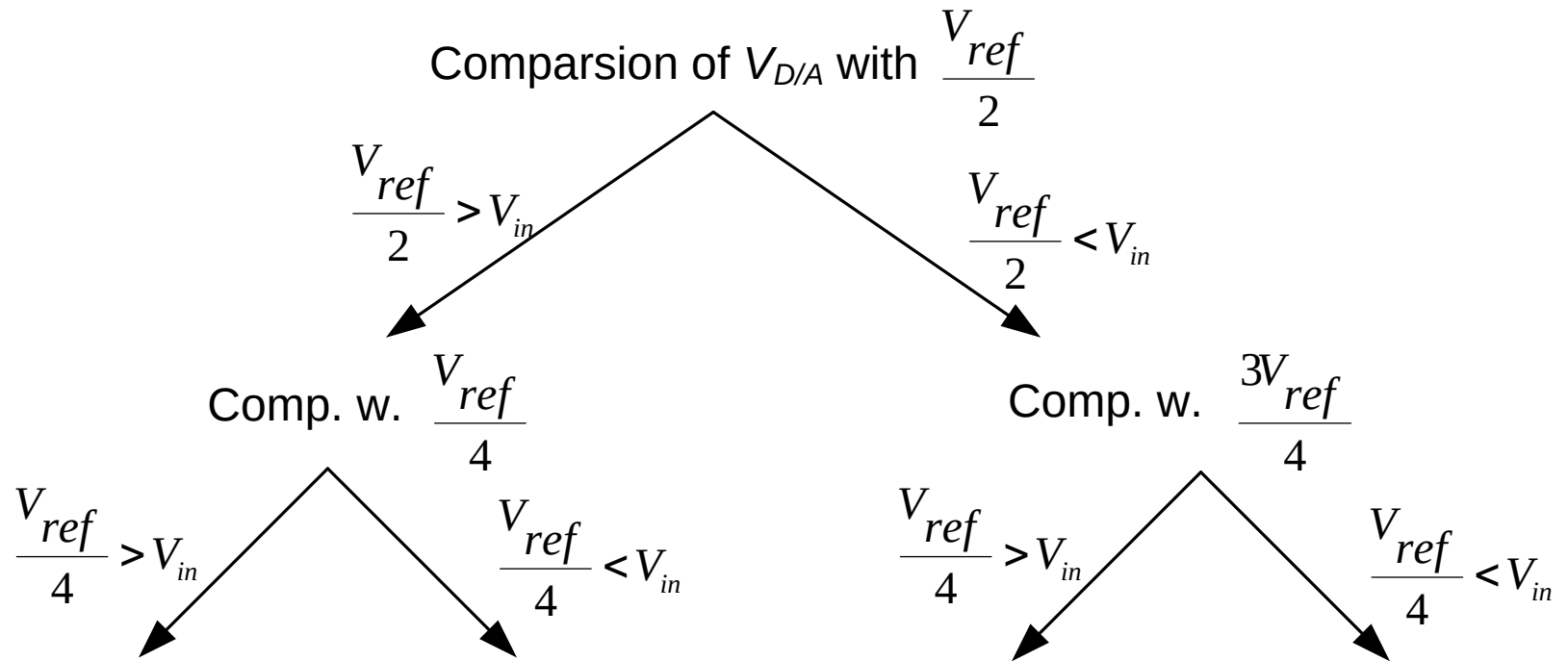

Successive Approximation ADC cont'd

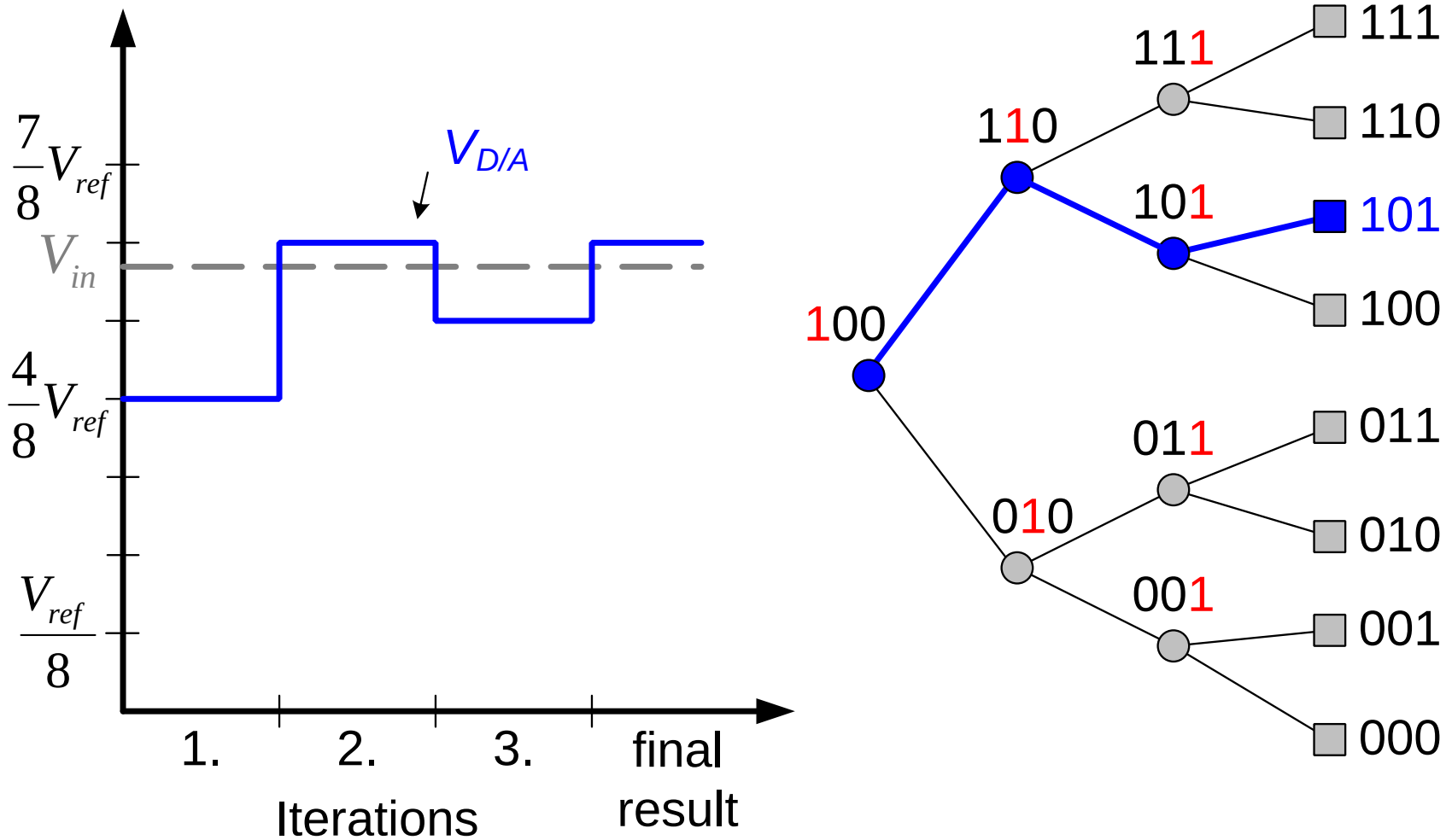


P. Fischer, VLSI-Design - ADC und DAC, Uni Mannheim, 2005

Successive Approx.: pros and cons


- ✓ Low Area / Low Power
- ✗ High effort for DAC
- ✗ Early wrong decision leads to false result

Algorithmic ADC

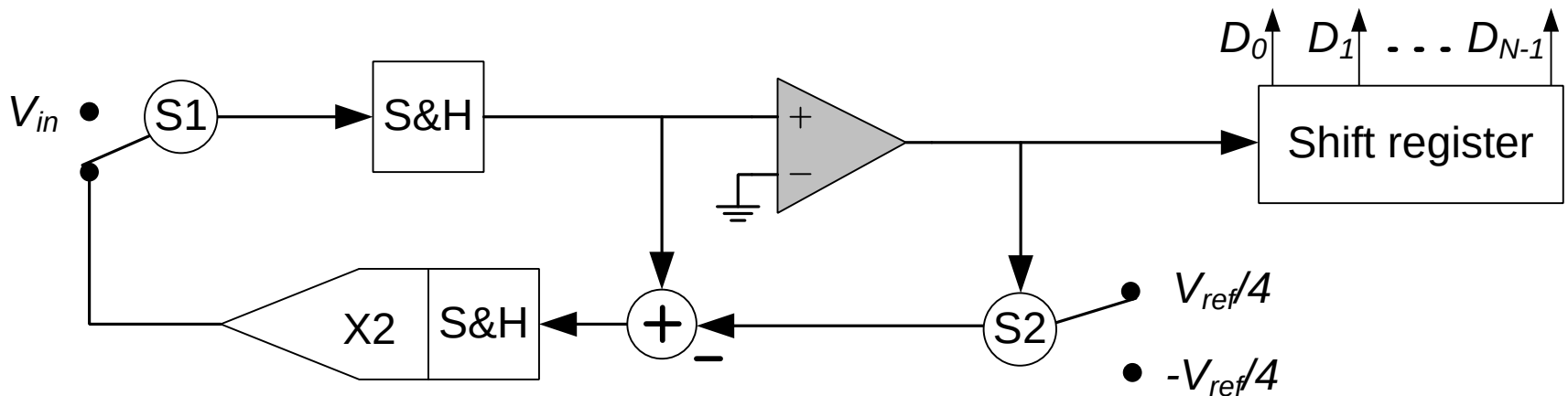- Same idea as successive approximation ADC
- Instead of modifying V_{ref} → doubling of error voltage (V_{ref} stays constant)



Algorithmic ADC con't

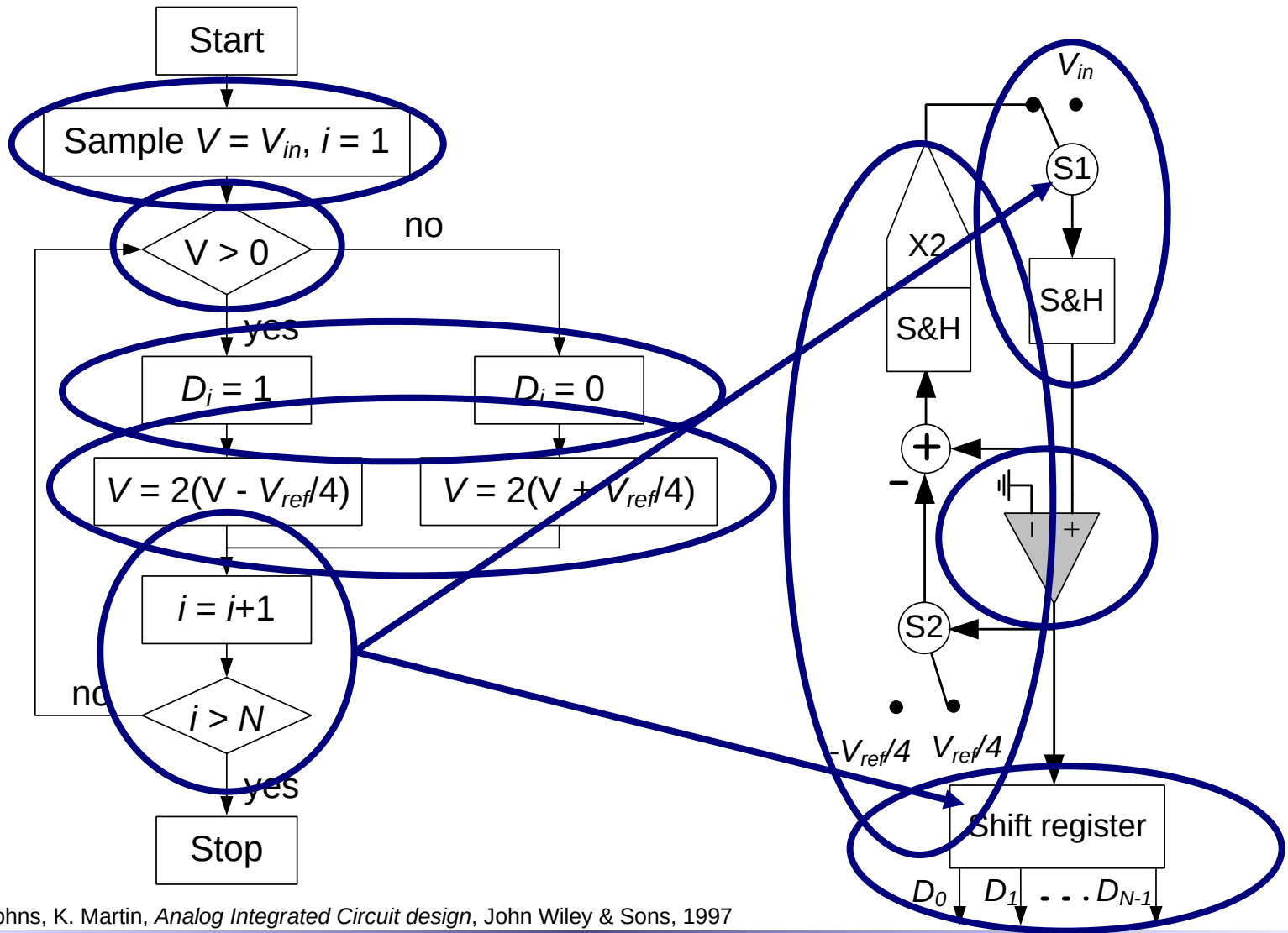


D.A.. Johns, K. Martin, *Analog Integrated Circuit design*, John Wiley & Sons, 1997

Algorithmic ADC: pros and cons

- ✓ Less analog circuitry than Succ. Approx. ADC
- ✓ Low Power / Low Area
- ✗ High effort for multiply-by-two gain amp

Flash ADC

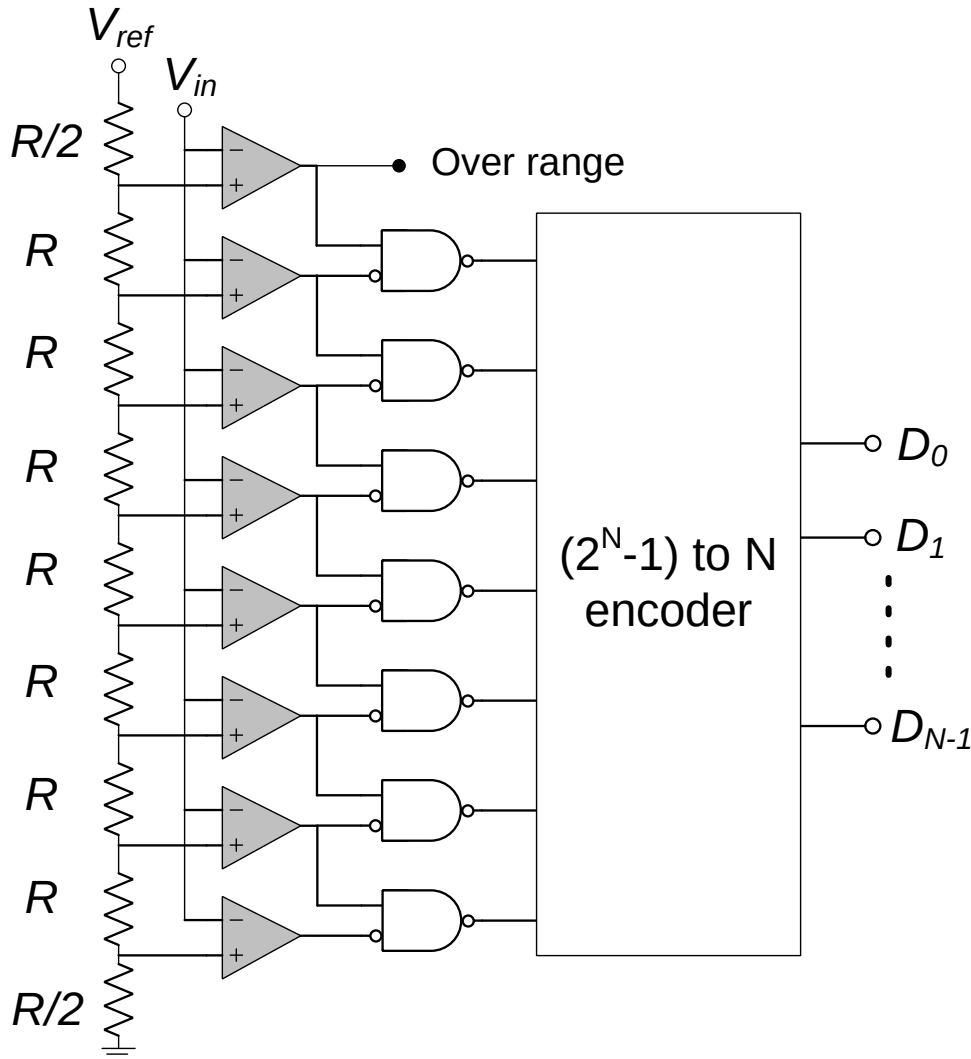

- V_{in} connected with 2^N comparators in parallel
- Comparators connected to resistor string
- Thermometer code
- $R/2$ -resistors on bottom and top for 0.5 LSB offset

Some Flash ADC design issues


- Input capacitive loading on V_{in}
- Switching noise if comparators switch at the same time
- Resistors-string bowing by input currents of bipolar comparators (if used)
- Bubble errors in the thermometer code based on comparator's metastability

Flash ADC: pros and cons

- ✓ Very fast
- ✗ High effort for the 2^N comparators
- ✗ High Area / High Power
- 👉 Recommended for 6-8 Bit and less

Two-Level Flash ADC

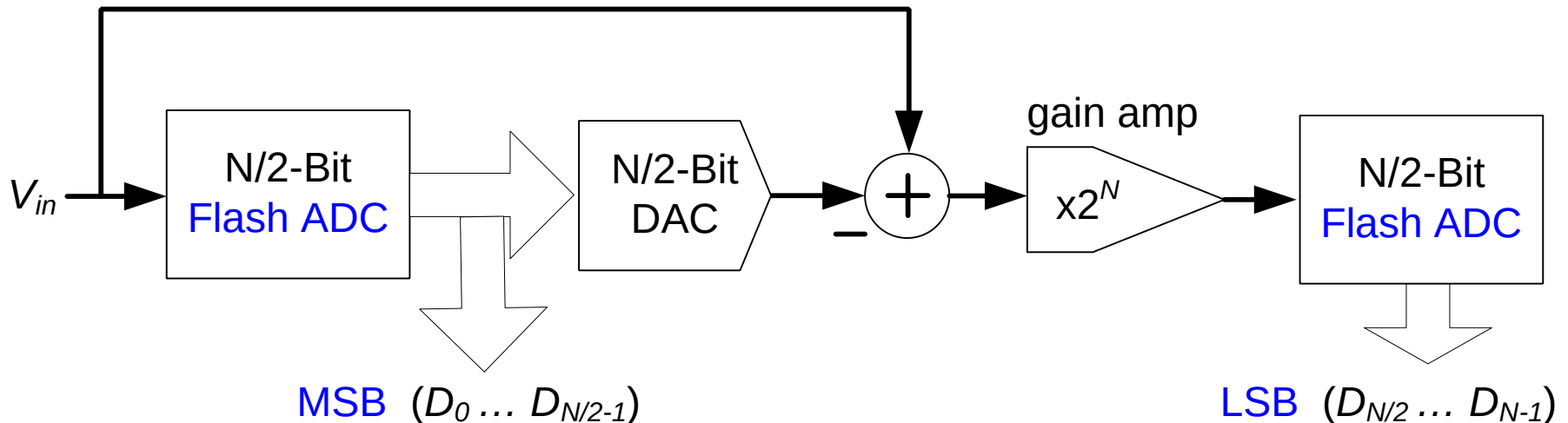- Conversion in two steps:
 1. Determination of MSB-Bits and reconvertng of digital signal by DAC
 2. Subtraction from V_{in} and determination of LSB-Bits
- F.e. 8-Bit-ADC: Flash: $2^8=256$ comparators, Two-level: $2 \cdot 2^4 = 32$ comparators




Two-Level Flash ADC: pros and cons


- ✓ Same throughput as Flash ADC
- ✓ Less area, less power, less capacity loading than Flash ADC
- ✓ Easy error-correction after first stage
- ✗ Larger latency delay than Flash ADC
- ✗ Design of $N/2$ -Bit-DAC
- ➡ Currently most popular approach for high-speed/medium accuracy ADCs

Pipelined ADCs

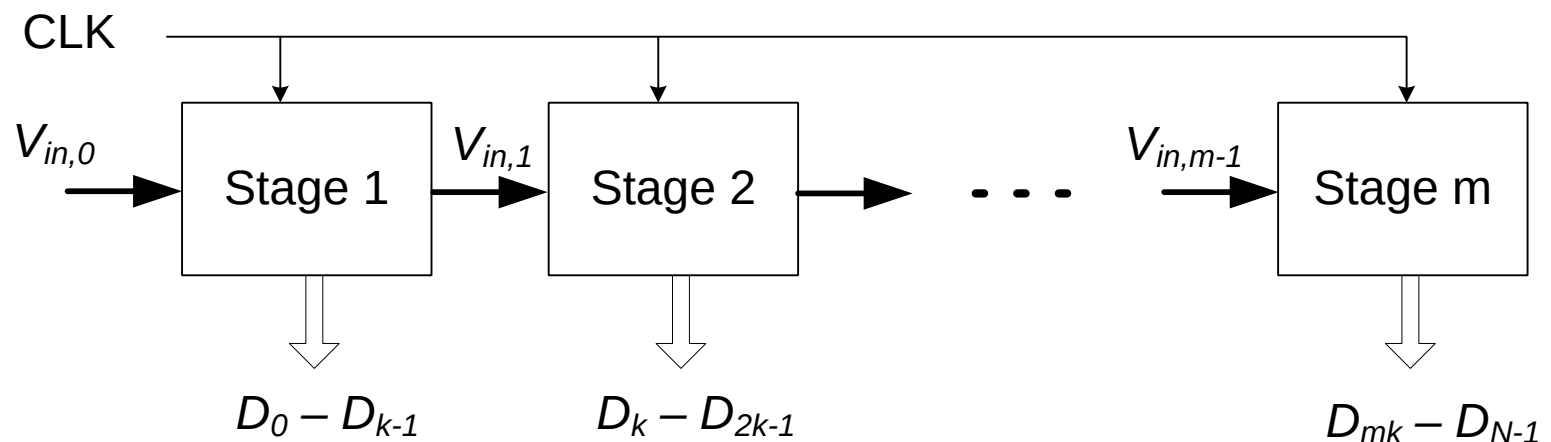- Extension of two-level architecture to multiple stages (up-to 1 Bit per stage)
- Each stage is connected with CLK-signal
 - ↳ Pipelined conversion of subsequent input signals
 - ↳ First result after m CLK cycles (m - amount of stages)
- Stages can be different



Pipelined ADCs: Scheme

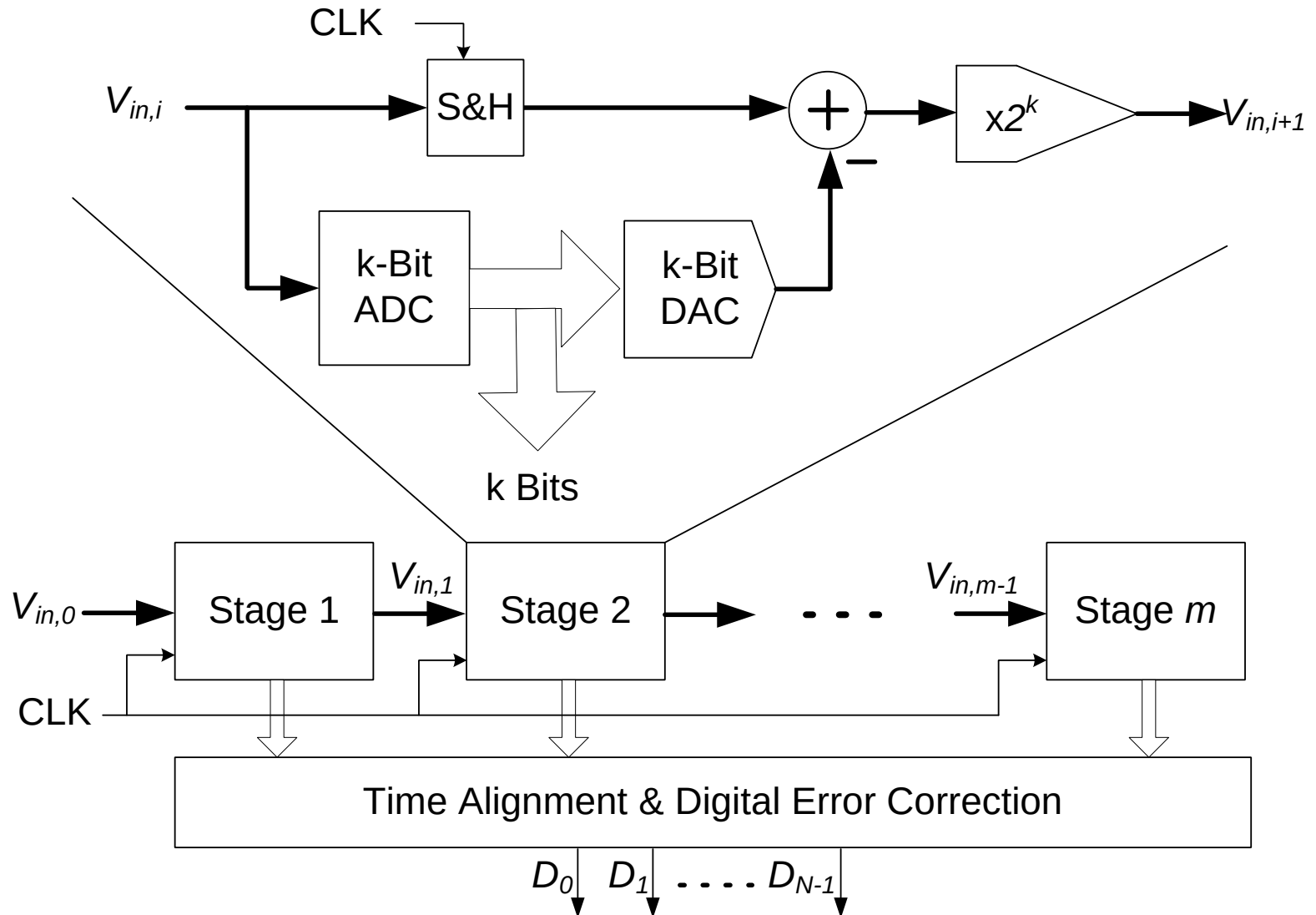


Pipelined ADC: pros and cons

- ✓ High throughput
- ✓ Easy upgrade to higher resolutions
- ✗ High demands on speed and accuracy on gain amplifier
- ✗ High CLK-frequency needed
- ✗ High Power


Oversampling (OS)

 - Quantized signal is low-pass filtered to frequency f_0
 - elimination of quantization noise greater than f_0




- Oversampling rate (OSR) is ratio of sampling frequency f_s to Nyquist rate of f_0
 - $$OSR = \frac{f_s}{2f_0}$$

Sigma Delta ADC Example

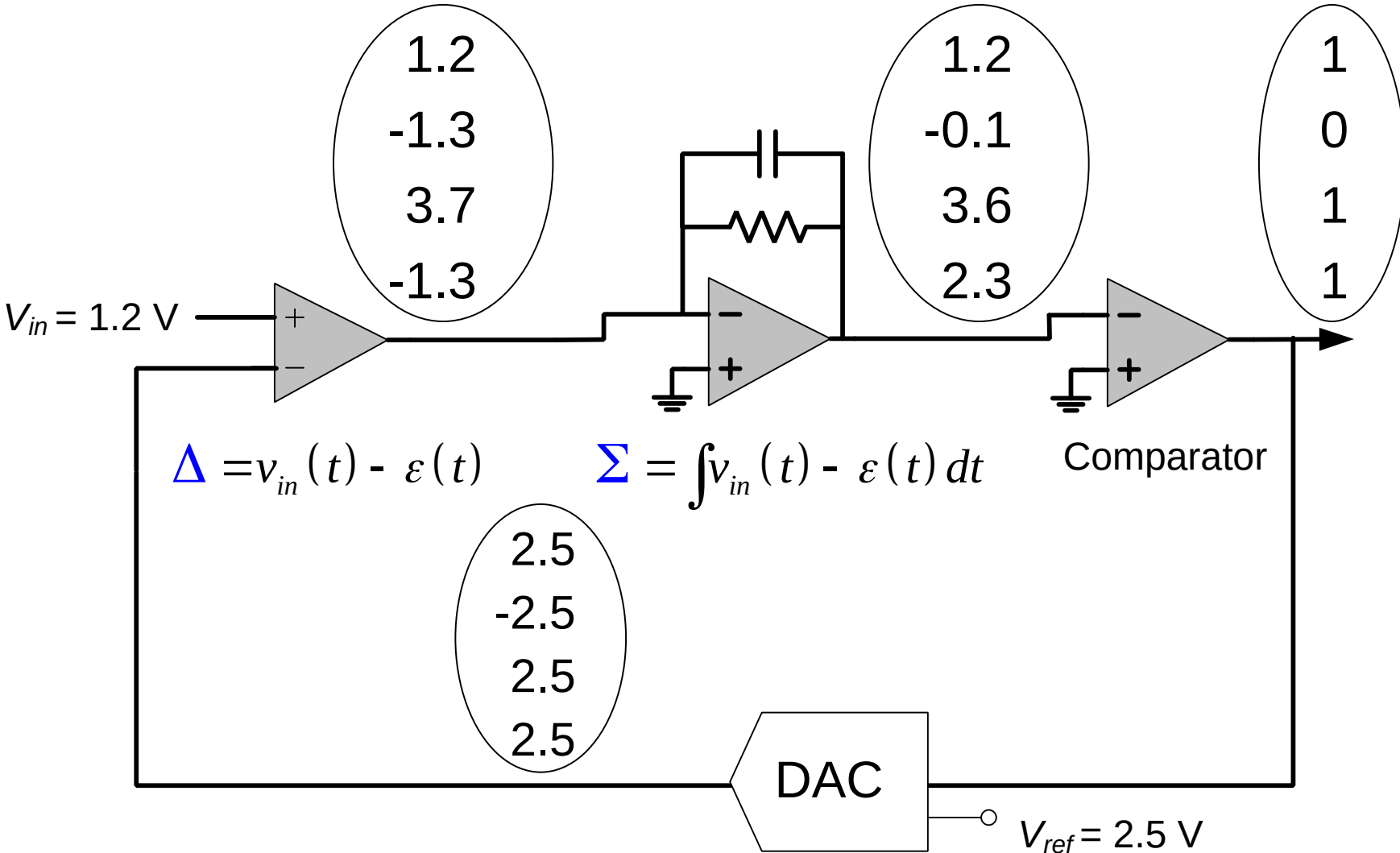

Sigma Delta ADC Example (Curves)

 

http://www.beis.de/Elektronik/DeltaSigma/DeltaSigma_D.html

Sigma Delta ADC: pros and cons

- ✓ High resolution
- ✓ Less effort for analog circuitry
- ✗ Low speed
- ✗ High CLK-frequency
- ↘ Currently popular for audio applications

5. Practical issues

- What are the performance limitations of ADCs?
- What are the differences between PCB- and IC-designs?
- Are there hints to improve the ADC design?
- What are S&H circuits?

Performance Limitations

Analog circuit performance limited by:

- High-frequency behavior of applied components
- Noise
 - Crosstalk (analog ↔ analog, analog ↔ digital)
 - Power supply coupling
 - Thermal noise (white noise)
- Parasitic components (capacitances, inductivities)
- Wire delays



PCB- versus IC-Design

- PCB: Printed Circuit Board, IC: Integrated Circuit
 - Noise in PCB-circuits much higher than in ICs
 - Influences of parasitics in PCB-circuits much higher than in ICs
 - High-frequency behavior of PCB-circuits much worse than of ICs
 - Wire delays in PCB much higher than in ICs
- ↳ *High accuracy, high speed, high bandwidth ADCs only possible in ICs!*

Some Hints for Mixed Signal Designs

For PCB and IC:

  - Keep ground lines separate!
- Don't overlap digital and analog signal wires!




Mancini, *Opamps for everyone*, Texas Instr., 2002

- Don't overlap digital and analog supply wires!
- Locate analog circuitry as close as possible to the I/O connections!
- Choose right passive components for high-frequency designs! (only PCB)

Sample and Hold Circuits

 - S&H circuits hold signal constant for conversion
- A sample and a hold device (mostly switch and capacitor)
- Demands:
 - Small RC-settling-time (voltage over hold capacitor has to be fast stable at < 1 LSB)
 - Exact switching point (else “aperture-error”)
 - Stable voltage over hold capacitor (else “droop error”)
 - No charge injection by the switch



6. Low Power ADC Design

- What are the main components of power dissipation?
- How can each component be reduced?
- What are the differences between power and energy?

Power Dissipation

Two main components:

- Dynamic power dissipation (P_{dyn})

- Based on circuit's activity
- Square dependency on supply voltage V_{DD}^2
- Dependent on clock frequency f_{clk}
- Dependent on capacitive load C_{load}
- Dependent on switching probability α

↳
$$P_{dyn} = V_{DD}^2 \cdot C_{load} \cdot f_{clk} \cdot \alpha$$

- Static power dissipation (P_{static})

- Constant power dissipation even if circuit is inactive
- Steady low-resistance connections between VDD und GND (only in some circuit technologies like pseudo NMOS)
- Leakage (critical in technologies $\leq 0.18 \mu\text{m}$)

Low Power ADC Design

- Reduction of V_{DD} :
 - Highest influence on power ($P \sim V_{DD}^2$)
 - Sadly, delay increases ($t_d \sim 1/V_{DD}$)
 - Sadly, loss of maximal amplitude → SNR goes down
 - Possible solutions:
 - Different supply voltages within the design
 - Dynamic change of V_{DD} depending on required performance
- Reduction of f_{clk} :
 - Dynamic change of f_{clk}

Low Power ADC Design cont'd

- Reduction of C_{load} :
 - C_{load} depends on transistor count and transistor size, wire count and wire length
 - Possible Solutions:
 - Reduction of amount evaluating components
 - Sizing of the design = all transistor get minimum size to reach desired performance
 - Intelligent placing and routing

Low Power ADC Design cont'd


- Reduction of α :

- Activity = possibility that a signal changes within one clock cycle

- Possible Solutions:

- Clock gating → no clock signal to inactive blocks

 - High active signals connected to the end of blocks



- Asynchronous designs



Which ADC for Low Power?

- If low speed: Dual Slope ADC
 - Area is independent of resolution
 - Less components
 - Problem: Counter
- If medium / high speed: mixed solutions
 - Popular: pipelined ADC with SAR
 - Pipelined solutions allows reduction of V_{DD}
 - Long latency but high throughput



Power vs. Energy

- Power consumption in Watts
 - Power = voltage · current at a specific time point
 - Peak power:
 - Determines power ground wiring designs and Packaging limits
 - Impacts of signal noise margin and reliability analysis
- Energy consumption in Joules
 - Energy = power · delay (joules = watts * seconds)
 - Rate at which power is consumed over time
 - Lower energy number means less power to perform a computation at the same frequency

Power vs. Energy cont'd

  

Power vs. Energy: Simple Example

 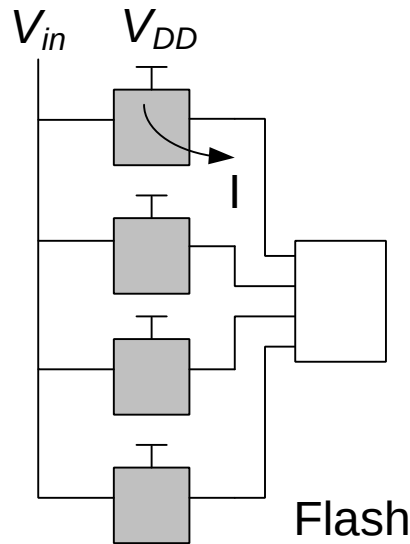

- Shaded blocks are ignored
- Dissipation for one input signal:

	V_{DD}	I (each gray block)	Delay	Power	Energy
Flash	1 V	1 μ A	1 ns	4 μ W	4 fJ
2L-Flash	1 V	1 μ A	2.5 ns	2 μ W	5 fJ

Low Power ADCs Conclusion

- There is **no patent solution** for low power ADCs!
- Every solution **depends on the specific task**.
- Before optimization **analyze the problem**:
 - Which resolution?
 - Which speed?
 - What are the constraints (area, energy, V_{DD} , V_{in} , ...)?
 - Which technology can be used?
- Think also about **unconventional solutions** (dynamic logic, asynchronous designs, ...).

Basic ADC Literature

- [All02] P. E. Allen, D. R. Holberg, "CMOS Analog Circuit Design", Oxford University Press, 2002
- [Azi96] P.M. Aziz, H. V. Sorensen, J. Van der Spiegel, "An Overview of Sigma-Delta Converters" IEEE Signal Processing Magazine, 1996
- [Eu07] E. D. Gioia, "Sigma-Delta-A/D-Wandler", 2007
- [Fi05] P. Fischer, "VLSI-Design 0405 - ADC und DAC", Uni Mannheim, 2005
- [Man02] Mancini, "Opamps for everyone", Texas Instr., 2002
- [Joh97] D. A. Johns, K. Martin, "Analog Integrated Circuit design", John Wiley & Sons, 1997
- [Tan00] S. Tanner, "Low-power architectures for single-chip digital image sensors", dissertation, University of Neuchatel, Switzerland, 2000.